

Canada Science and Technology Museum

Name:

Date:

Will these circuits work?



1



2



3



4



5



6